

5.5.3 VHDL语言的描述风格

三种描述风格:

行为描述: 使用功能描述

数据流(寄存器传输): 使用布尔代数式描述

结构描述: 模块间的连接关系描述

5.5.4 基本逻辑电路的VHDL设计

一、组合电路

原则1： 在process中用到的所有输入信号都出现在敏感信号列表中；

原则2： 电路的真值表必须在代码中完整的反映出来。（否则会生成锁存器）

原则3： 使用if · · else · · ，必须完全互斥。

1. 三态门及总线缓冲器

——指定大写“Z”表示高阻态

```
a <= 'Z' ;
```

```
a_bus <= "ZZZZZZZZ" ;
```

```



LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.all;

ENTITY tri_gate IS
    port ( din, en: IN std_logic;
          dout: OUT std_logic );
END tri_gate;

ARCHITECTURE art OF tri_gate IS
BEGIN
    PROCESS (din, en)
    BEGIN
        IF (en= '0' ) then
            dout <= din;
        ELSE
            dout<= 'Z' ;
        END IF;
    END PROCESS
END art;

```

8位数据总线?

  


2. 8:3优先编码器

```
library ieee;
use ieee.std_logic_1164.all;

ENTITY priencoder is
PORT (input:IN STD_LOGIC_VECTOR(7 downto 0);
      ei:IN STD_LOGIC;
      yout:OUT STD_LOGIC_VECTOR(2 downto 0);
      eo,gs:OUT STD_LOGIC);
END priencoder;

 ARCHITECTURE cod74148 OF priencoder IS
BEGIN
  PROCESS(ei,input)
  BEGIN
    IF(ei='1')THEN
      yout <= "111";
      eo <= '1';
      gs <= '1';
    ELSE
```



输 入									输 出			
$\overline{E_I}$	\bar{I}_7	\bar{I}_6	\bar{I}_5	\bar{I}_4	\bar{I}_3	\bar{I}_2	\bar{I}_1	\bar{I}_0	\bar{Y}_2	\bar{Y}_1	\bar{Y}_0	$\overline{G_s} \overline{E_o}$
1	×	×	×	×	×	×	×	×	1	1	1	1 1
0	1	1	1	1	1	1	1	1	1	1	1	1 0
0	0	×	×	×	×	×	×	×	0	0	0	0 1
0	1	0	×	×	×	×	×	×	0	0	1	0 1
0	1	1	0	×	×	×	×	×	0	1	0	0 1
0	1	1	1	0	×	×	×	×	0	1	1	0 1
0	1	1	1	1	0	×	×	×	1	0	0	0 1
0	1	1	1	1	1	0	×	×	1	0	1	0 1
0	1	1	1	1	1	1	0	×	1	1	0	0 1
0	1	1	1	1	1	1	1	0	1	1	1	0 1

输 入									输 出			
$\overline{E_I}$	\bar{I}_7	\bar{I}_6	\bar{I}_5	\bar{I}_4	\bar{I}_3	\bar{I}_2	\bar{I}_1	\bar{I}_0	\bar{Y}_2	\bar{Y}_1	\bar{Y}_0	$\overline{G_sE_o}$
1	×	×	×	×	×	×	×	×	1	1	1	1 1
0	1	1	1	1	1	1	1	1	1	1	1	1 0
0	0	×	×	×	×	×	×	×	0	0	0	0 1
0	1	0	×	×	×	×	×	×	0	0	1	0 1
0	1	1	0	×	×	×	×	×	0	1	0	0 1
0	1	1	1	0	×	×	×	×	0	1	1	0 1
0	1	1	1	1	0	×	×	×	1	0	0	0 1
0	1	1	1	1	1	0	×	×	1	0	1	0 1
0	1	1	1	1	1	1	0	×	1	1	0	0 1
0	1	1	1	1	1	1	1	0	1	1	1	0 1

```
IF (input(7)='0')THEN
```

```
    yout <= "000";
```

```
    eo <= '1' ;
```

```
    gs <= '0' ;
```

```
ELSIF (input(6)='0')THEN
```

```
    yout <= "001";
```

```
    eo <= '1' ;
```

```
    gs <= '0' ;
```

```
ELSIF (input(5)='0')THEN
```

```
    yout <= "010";
```

```
    eo <= '1' ;
```

```
ELSIF (input(0)='0')THEN
```

```
    yout <= "111";
```

```
    eo <= '1' ;
```

```
    gs <= '0' ;
```

```
ELSE yout <= "111";
```

```
    eo <= '0' ;
```


```
    gs <= '1' ;
```

```
END IF;
```

```
END IF;
```

```
END PROCESS;
```

```
END cod74148;
```

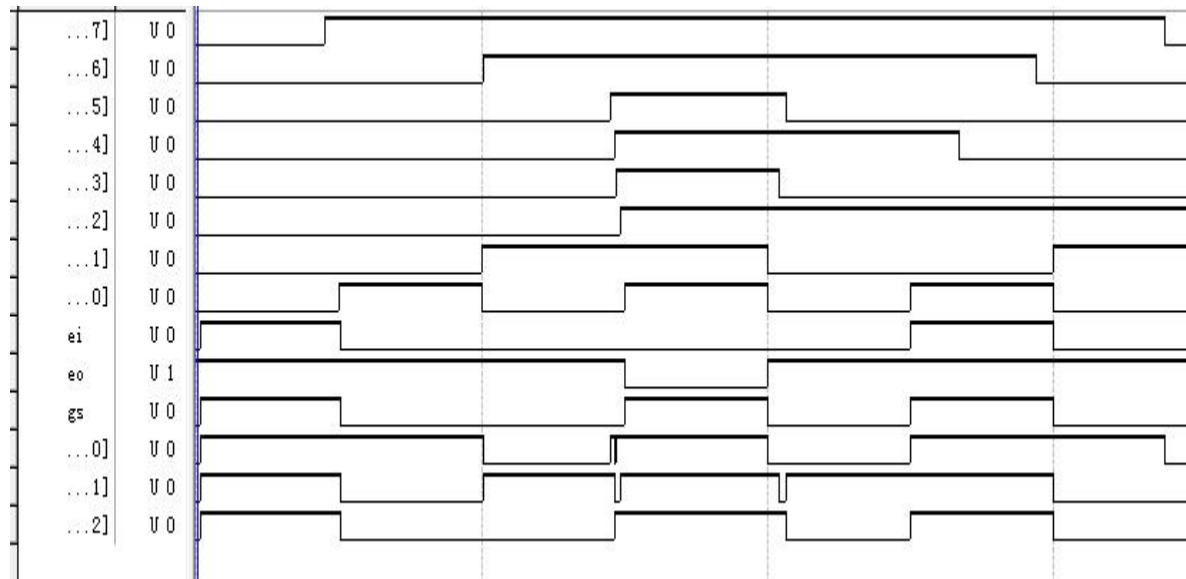

输 入									输 出			
$\overline{E_I}$	$\overline{I_7}$	$\overline{I_6}$	$\overline{I_5}$	$\overline{I_4}$	$\overline{I_3}$	$\overline{I_2}$	$\overline{I_1}$	$\overline{I_0}$	$\overline{Y_2}$	$\overline{Y_1}$	$\overline{Y_0}$	$\overline{G_s E_o}$
1	×	×	×	×	×	×	×	×	1	1	1	1 1
0	1	1	1	1	1	1	1	1	1	1	1	1 0
0	0	×	×	×	×	×	×	×	0	0	0	0 1
0	1	0	×	×	×	×	×	×	0	0	1	0 1
0	1	1	0	×	×	×	×	×	0	1	0	0 1
0	1	1	1	0	×	×	×	×	0	1	1	0 1
0	1	1	1	1	0	×	×	×	1	0	0	0 1
0	1	1	1	1	1	0	×	×	1	0	1	0 1
0	1	1	1	1	1	1	0	×	1	1	0	0 1
0	1	1	1	1	1	1	1	0	1	1	1	0 1

二、时序逻辑电路设计

触发器、寄存器、计数器、分频器、节拍发生器、状态机等。

进程的敏感信号是时钟信号，在进程内部用if语句描述时钟的边沿条件。

时钟上升沿：

(clock'event and clock = '1')

时钟下降沿：

(clock'event and clock = '0')

敏感信号表的特点:

1) 敏感信号表中只有时钟信号——同步复位等。

如:

```
process (clk)
begin
    if (clk' event and clk = '1' )
then
        if reset = '1' then
            data <= "00" ;
        else
            data <= in_data;
        end if;
    end if;
end process;
```

最先判断时钟



同步复位



同步复位2D触发器

2) 敏感信号表中除时钟外，还有其它信号——异步操作

例：

```
process (clk, reset)
```

最先判断异步复位

```
begin
```

```
    if reset = '1' then
```

```
        data <= "00" ;
```

```
    elsif (clk' event and clk = '1' ) then
```

```
        data <= in_data;
```

```
    end if;
```

```
end process;
```

对于判断时钟电路边沿，
后没有“else”语句。

同步、异步区别：敏感信号表、语句顺序

2) 计数器

描述计数器 (`std_logic_vector`), 要用到中间信号和标准的程序包: `IEEE.STD_LOGIC_UNSIGNED`

例: 异步置数(低有效) 的10进制计数器。

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity counter10 is
    Port ( clk : in std_logic;
          load : in std_logic;
          din : in std_logic_vector(3 downto 0);
          qout : out std_logic_vector(3 downto 0);
          c: out std_logic);
end counter10;
```

architecture art of counter10 is

signal temp : std_logic_vector(3 downto 0);

begin

process (clk, load, din)

begin

if (load= '0') then

temp <= din;

elsif (clk'event and clk= '1') then

if (temp = "1001") then

--if (temp=9) then

temp <= "0000";

else

temp <= temp+1;

end if;

end if;

end process;

qout <= temp;


c <= '1' when temp="1001" else


'0';

--when temp=9 else

end art;

为描述计数过程，
定义中间信号。

 

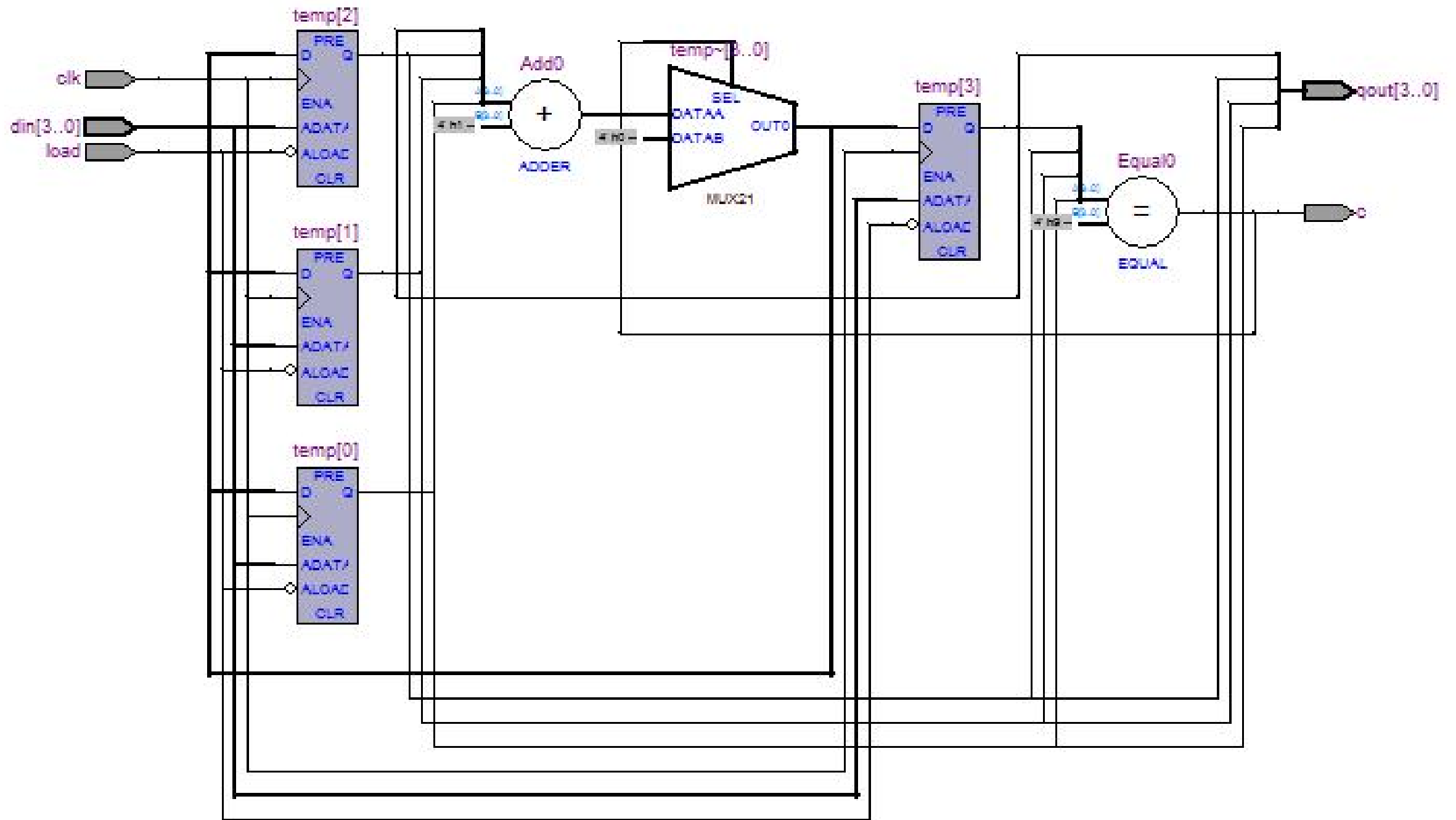

```
.....
process (clk, reset, din)
begin
```


```
    if (load= '0' ) then
        temp <= din;
```


```
    elsif (clk'event and clk= '1') then
        if (temp = 9) then
            temp <= "0000";
            c <= '1';
        else
            temp <= temp+1;
            c <= '0';
        end if;
```

```
    end if;
end process;
qout <= temp;
End art
```

```
if (clk'event and clk= '1') then
    if (temp = m-1) then
        temp <= "00...00";
    else
        temp <= temp+1;
    end if;
end if ;
end process ;

 q <= temp;
c <= '1' when temp=m-1 else
    '0';
```



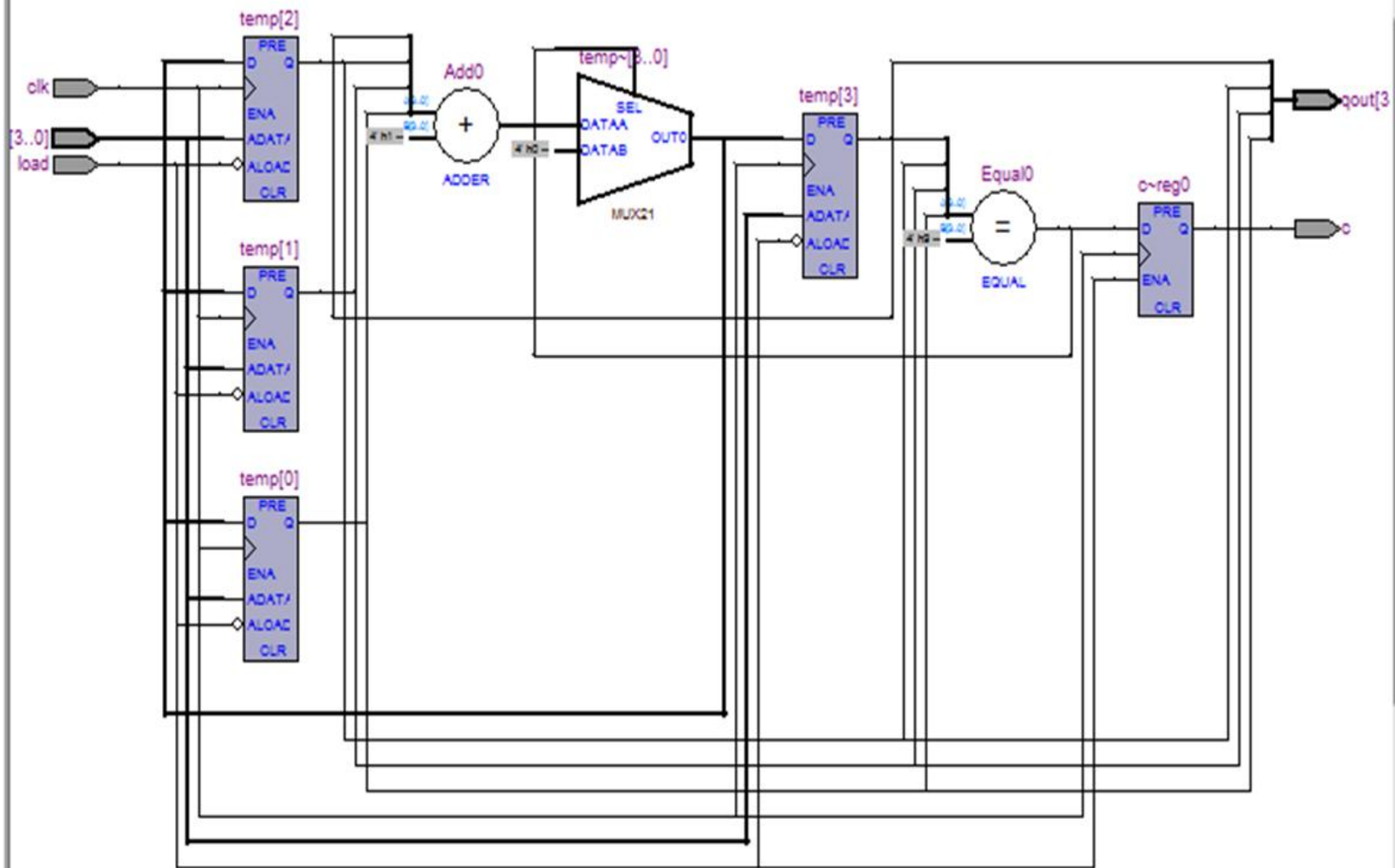

例：六十进制（分、秒）计数器

与一般二进制计数器不同，分个位十位显示，为分、秒计数

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity clock60 is
```

```
    Port ( clk : in std_logic;
```

```
          clr : in std_logic;
```

```
          s1 : out std_logic_vector(3 downto 0);
```

```
          s10 : out std_logic_vector(2 downto 0);
```

```
          co : out std_logic );
```

```
end clock60;
```

```
architecture art of clock60 is
```

```
    signal s1_temp : std_logic_vector(3 downto 0);
```

```
    signal s10_temp : std_logic_vector(2 downto 0);
```



88

begin

```
process (clk, clr)
```

begin

```
if (clr= '1') then
```

```
s1_temp <= "0000";
```

```
s10_temp <= "000";
```

```
elseif (clk'event and clk= '1') then
```

```
if (s1_temp= 9) then
```

```
s1_temp<= "0000";
```

```
if (s10_temp = 5) then
```

```
s10_temp<= "000";
```

else

```
s10_temp <= s10_temp+1;
```

end if;

else

```
s1_temp <= s1_temp+1;
```

end if;

end if;


```
end process;
```

```
s1 <= s1_temp;
```

```
s10 <= s10_temp;
```

```
co <= '1' when ( s10_temp=5 and s1_temp=9) else
    '0';
```

End art;

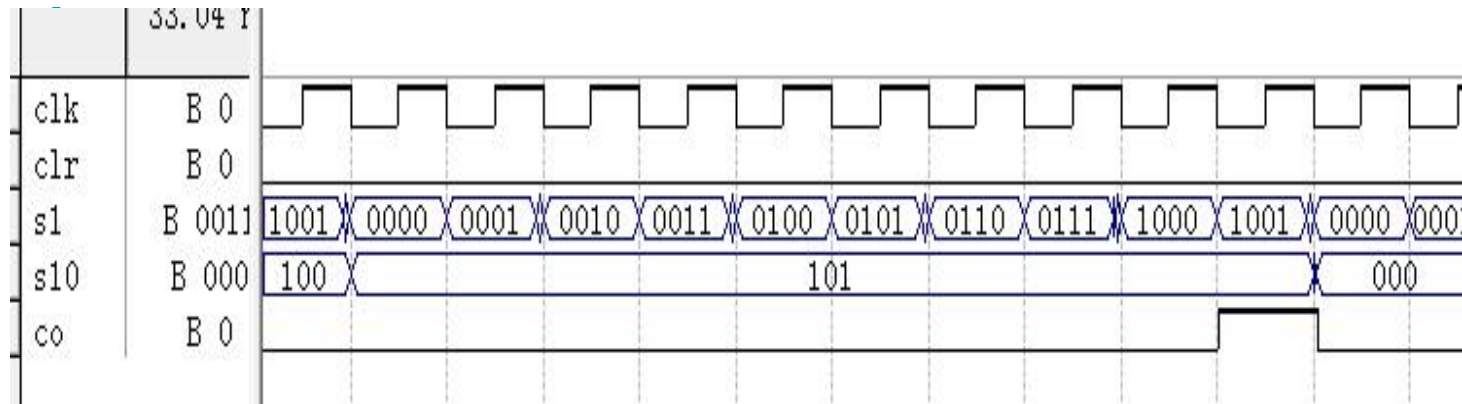

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```

模可控计数器（由输入x, y控制）

M=3,4,6,7

```
ENTITY add IS  
  PORT(clk, x,y:IN STD_LOGIC;  
        qout: OUT STD_LOGIC_VECTOR (2 DOWNT0 0);  
        co:OUT STD_LOGIC);  
END add;
```

```
ARCHITECTURE behv OF add Is  
  SIGNAL con : std_logic_vector (1 downto 0);  
  SIGNAL temp : std_logic_vector (2 downto 0);  
  SIGNAL m : integer range 7 downto 0;  
BEGIN
```

PROCESS(x,y) -- 组合逻辑

```
begin  
  con<=x&y;  
  case con is  
    when "00" => m<= 3 ;  
    when "01" => m<= 4;  
    when "10" => m<= 6;  
    when others => m<= 7;  
  END case;
```


END process;

PROCESS (clk, m) – 时序逻辑

```
begin  
  if (clk'event and clk='1') then  
    if (temp = m-1) then  
      temp <= "000";  
    else  
      temp <=temp+1;  
    END IF;  
  END IF;  
END PROCESS;
```

```
qout <= temp ;  
co <= '1' when temp=m-1 else  
  '0';
```

END behv;

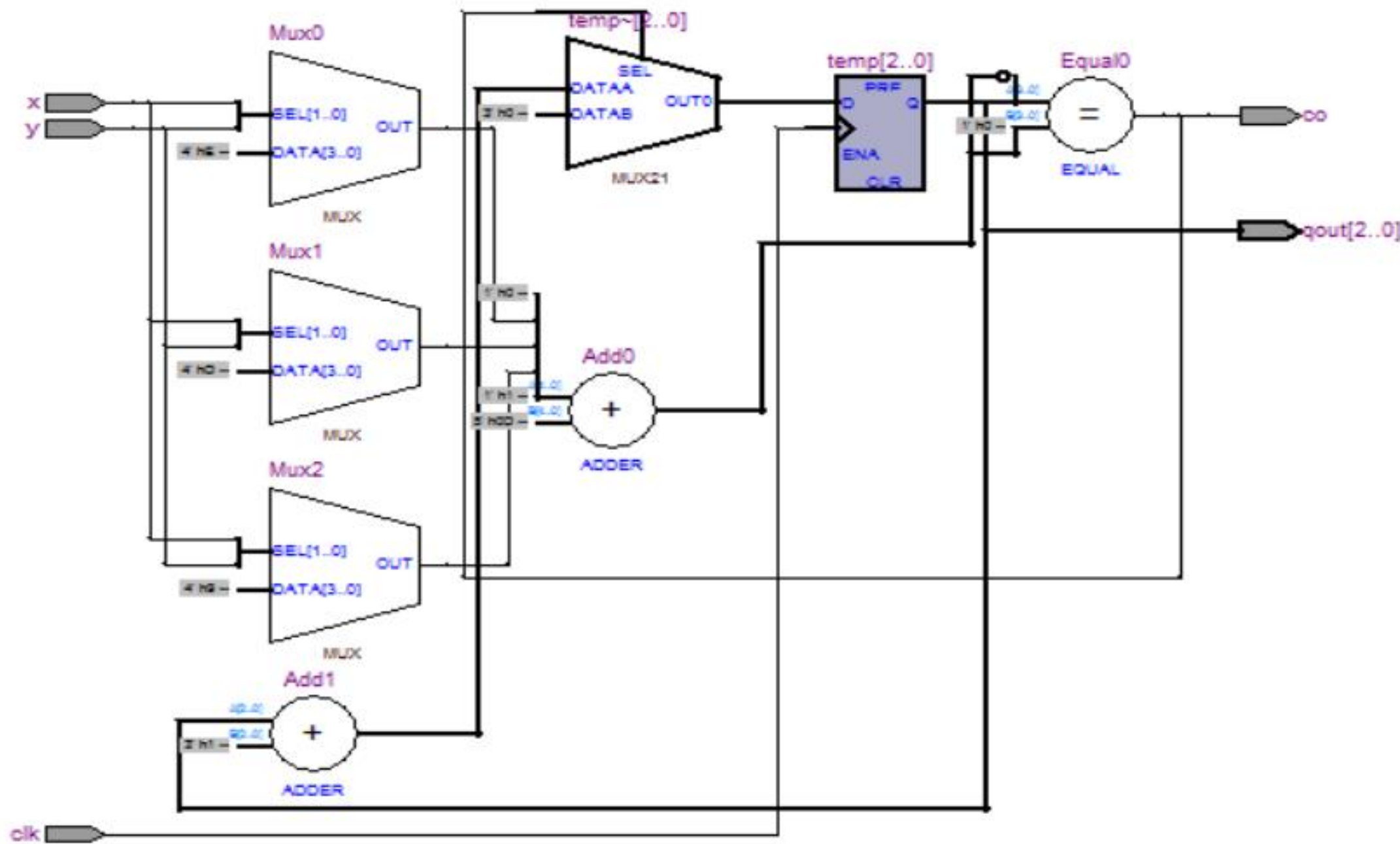

例：设计5000分频器

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity fp is  
    Port ( clk : in std_logic;  
          clkout : out std_logic);  
end fp;
```

```
architecture art of fp is  
    signal temp: integer range 0 to 4999;  
Begin
```

```
process (clk)
begin
    if (clk' event and clk= '1' ) then
        if ( temp=4999) then
            temp <= 0 ;
        else
            temp <= temp+1;
        end if;
    end if;
```

```
end process;
```

```
process ( clk , temp)
begin
```



```
    if (clk' event and clk= '1' ) then
        if( temp<2500) then clkout <= '1' ;
        else                clkout <= '0';
        end if;
```

```
    end if;
```

```
End process;
```

```
end art;
```

(方波)

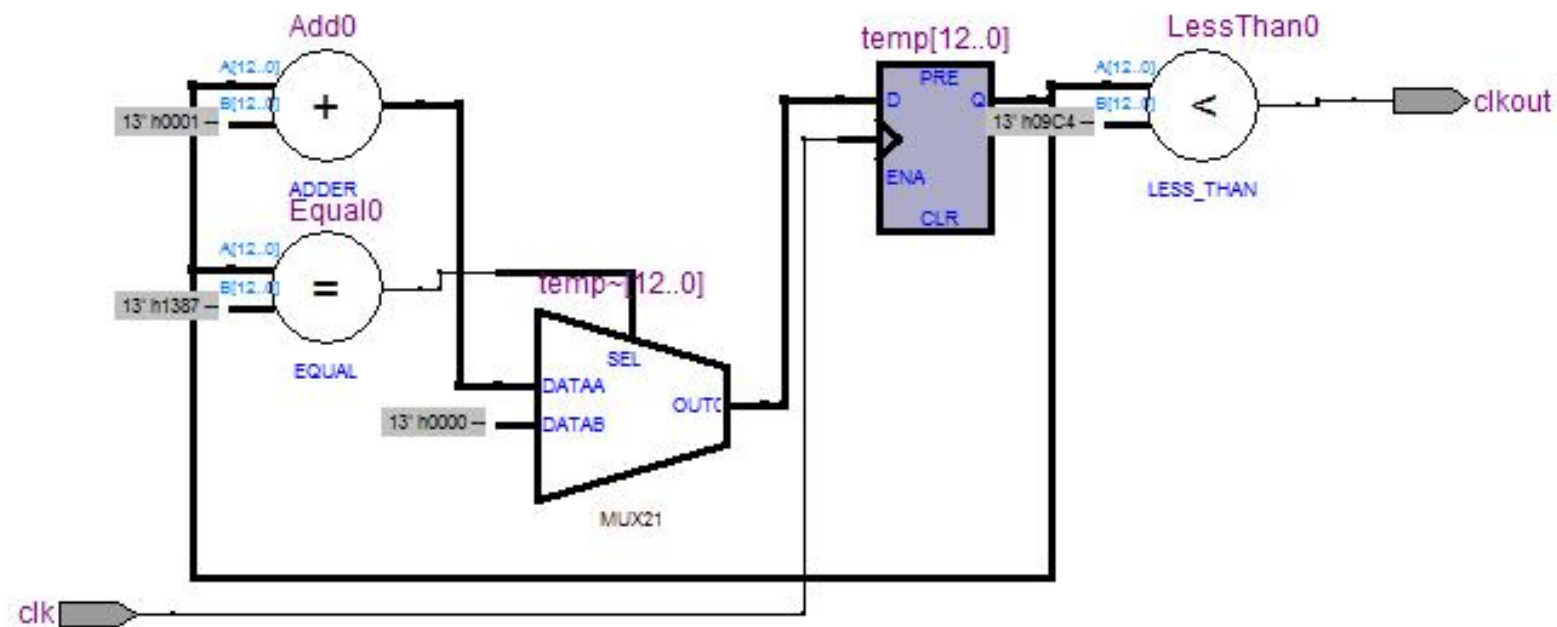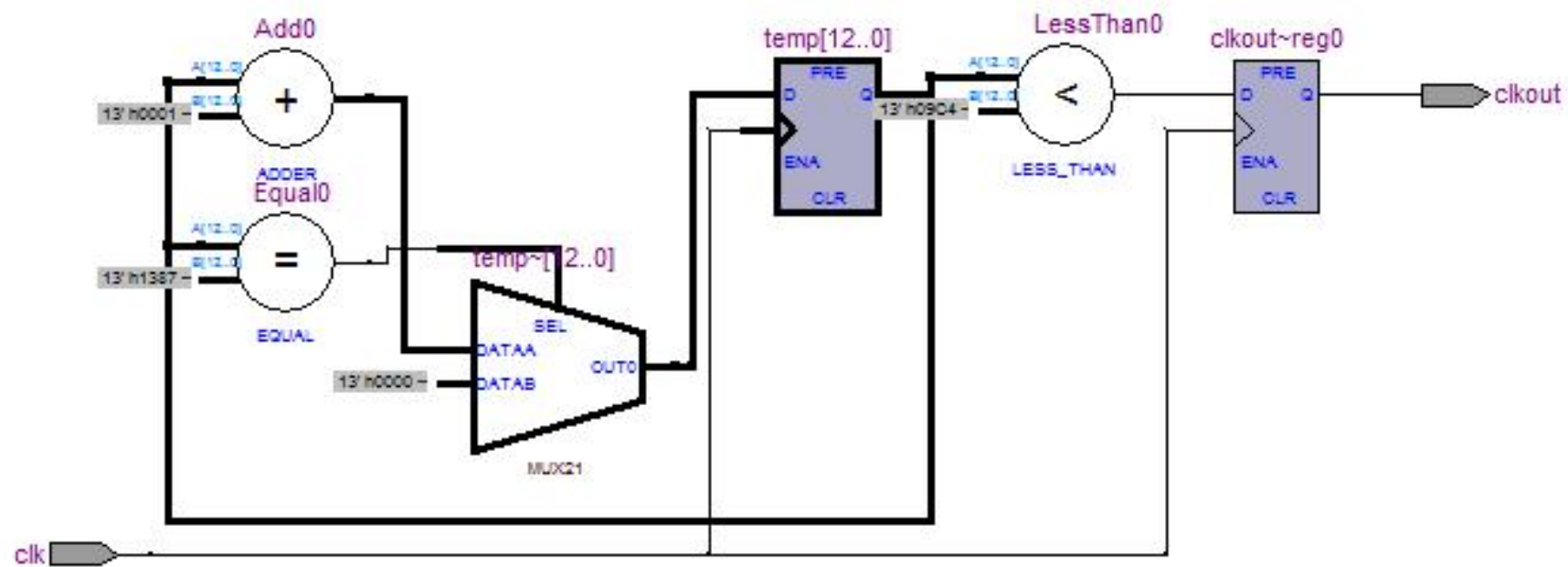

例：8位环形移位寄存器（左、右移、异步置数）

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity shfirt is
    Port ( clk ,load,con: in std_logic;
           din: in std_logic_vector (7 downto 0);
           qout : out std_logic_vector (7 downto 0)
         );
end shfirt;

architecture art of shfirt is
    signal q_temp: std_logic_vector (7 downto 0);
begin
```

```
process (clk, load, din, con)
begin
    if load= '1' then
        q_temp <= din;
    elsif (clk' event and clk= '1' ) then
        if con= '1' then
            q_temp <= q_temp (6 downto 0) & q_temp(7) ;
        else
            q_temp <= q_temp(0) & q_temp (7 downto1);
        end if;
    end if;

End process;
qout <= q_temp;
End art;
```


例：环型顺序脉冲发生器(4位)

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity index is  
    Port ( clk ,ld: in std_logic;  
          y : out std_logic_vector (3 downto 0)  
          );  
end index;  
  
architecture art of index is  
    signal q: std_logic_vector (3 downto 0);  
begin
```


```

process (clk)
begin
    if (clk' event and clk= '1' )    then
        if ld= '0'  then
            q <= "1000"  ;
        else
            q <= q (0) & q (3 downto 1);
        end if;
    end if;
End process;

```

End art;

y <= q ;

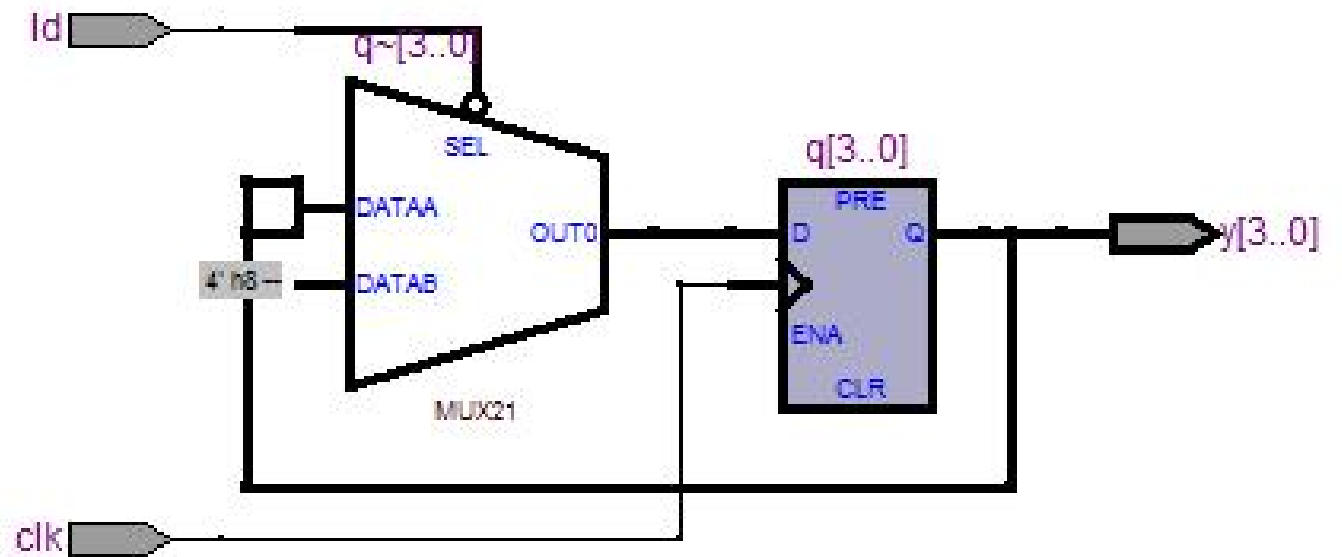

3) 状态机

- 用户自定义数据类型

利用用户自定义数据类型——枚举类型实现。

语法格式：

```
type 数据类型名 is 数据类型定义（枚举）；
```

综合器自动实现枚举类型元素的编码

```
type week is (sun, mon, tue, wed, thu,  fri, sat);  
Signal day : week ;  
      .....  
      day <= sun;
```

```
type statetype is (s0, s1, s2, s3);  
signal present_state, next_state : statetype;  
      .....  
      present_state <= S0 ;
```

• 状态转移的描述

CASE 现态 IS

WHEN 表达式值1 => 顺序处理语句11; 语句12;

.....

WHEN 表达式值3 => 顺序处理语句31; 语句32;


END CASE;

• 状态机整体描述结构和输出的描述

组合进程：描述状态逻辑、输出逻辑；

时序进程：描述从次态到现态转换；

—— 两段式有限状态机

 


Moore 型状态机的描述

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY moore IS
    PORT ( clk, x : IN STD_LOGIC;
          y: OUT STD_LOGIC );
END moore;

ARCHITECTURE behv OF moore IS
    TYPE State IS (s0, s1, s2, s3);
    SIGNAL current_state, next_state: State;
BEGIN

     PROCESS (clk) -- 时序逻辑
    BEGIN
        IF (clk'EVENT and clk='1' ) THEN
            current_state <= next_state;
        END IF ;
    END PROCESS;
```



第一进程，完成状态转换，
必须饱含时钟敏感信号

PROCESS (current_state, x) — 组合逻辑
BEGIN

CASE current_state **IS**

WHEN s0 => y <= '0';

IF x = '0' **THEN**

next_state <= s0;

ELSE

next_state <= s1;

END IF;

WHEN s1 => y <= '1';

IF x = '0' **THEN**

next_state <= s2;

ELSE

next_state <= s1;

END IF;

WHEN s2 => y <= '0';

IF x = '0' **THEN**

next_state <= s3;

ELSE

next_state <= s2;

END if;

摩尔型

第二进程：输出和状态逻辑间关系，必须包含现态、输入等敏感信号

WHEN s3 => y <= '0';

IF x = '0' **THEN**

next_state <= s1;

ELSE


next_state <= s0;

END IF;

END CASE;

END process;

END behy;

 


Mealy 型有限状态机的设计

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY mealy IS
    PORT ( clk , x : IN STD_LOGIC;
          y: OUT STD_LOGIC );
END mealy;

 ARCHITECTURE behv OF mealy IS
    TYPE state IS (s0, s1, s2, s3);
    SIGNAL current_state, next_state: state;
BEGIN
    PROCESS (clk)
    BEGIN
        IF (clk'EVENT and clk='1' ) THEN
            current_state <= next_state;
        END IF ;
    END PROCESS;
END mealy;
```



PROCESS (current_state, x)

BEGIN

CASE current_state **IS**

WHEN s0 => **IF** x = '0' **THEN**

next_state <= s0;

y <= '0';

ELSE

next_state <= s1;

y <= '0';

END IF;

WHEN s1 => **IF** x = '0' **THEN**

next_state <= s0;


y <= '0';

ELSE

next_state <= s2;

y <= '0';

END IF;

 

WHEN s2 => **IF** x = '0' **THEN**

next_state <= s0;

y <= '0';

ELSE

next_state <= s3;

y <= '0';

END IF;

WHEN s3 => **IF** x = '0' **THEN**

next_state <= s0;

y <= '1';

ELSE

next_state <= s3;



y <= '0';

END IF;

END case;

END PROCESS;


END behv;

  

5.5.4 VHDL的层次化（结构化）设计与元件例化(component)语句

在多层次的设计中，高层次的设计模块调用低层次的设计模块，构成模块化的设计。重点描述模块间的连接关系。

由元件声明、元件例化两部分关键语句组成。

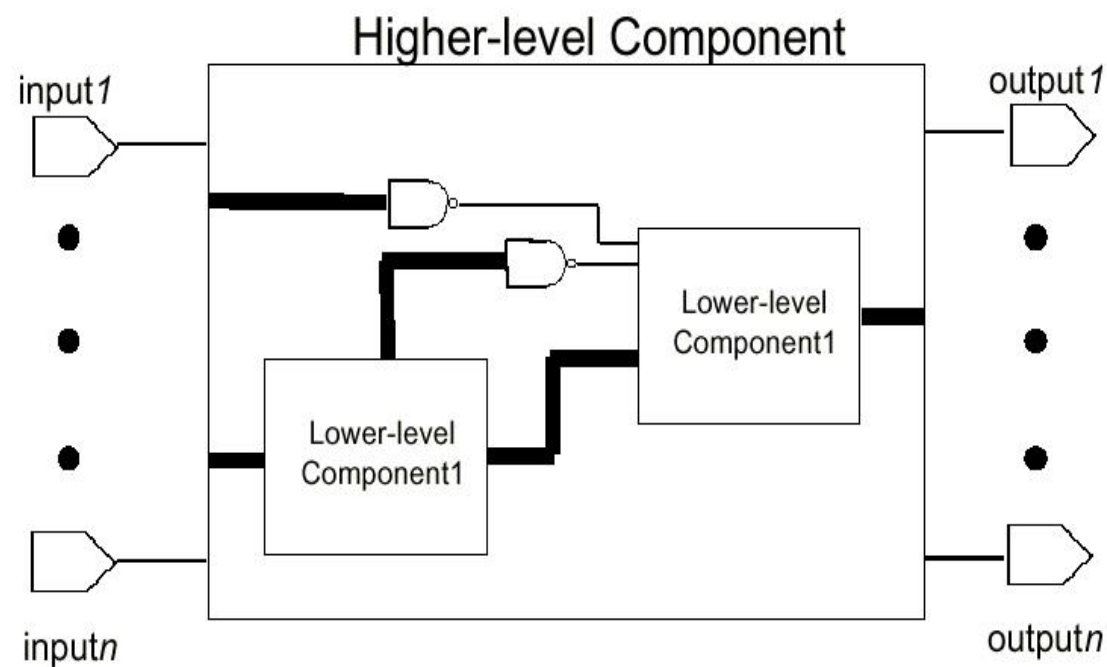

被例化元件的来源:

- VHDL设计实体;
- 其它HDL设计实体;
- 厂商提供的工艺库中的元件、IP核。

层次化设计的优点:

- 分工
- 共享
- 移植
- 周期短

一个元件是一段结构完整的常用代码，包括声明，实体和结构体，使用component可以使代码具有层次化的结构。

1. **元件声明**：在结构体说明区中对所调用的低层次的实体模块（名称、端口类型等）声明为元件。

语 法 格 式：

```
COMPONENT 元件名  
    PORT (端口名表) ;  
END COMPONENT ;
```


2. **元件例化**：将低层次元件调用、安装到当前层次。给出连接映射。

语 法 格 式：

```
例化名：低层元件名 PORT MAP ( 端口列表) ;
```

端口列表：低层端口名=> 当前名称
(或，直接位置映射)

一位全加器原理图

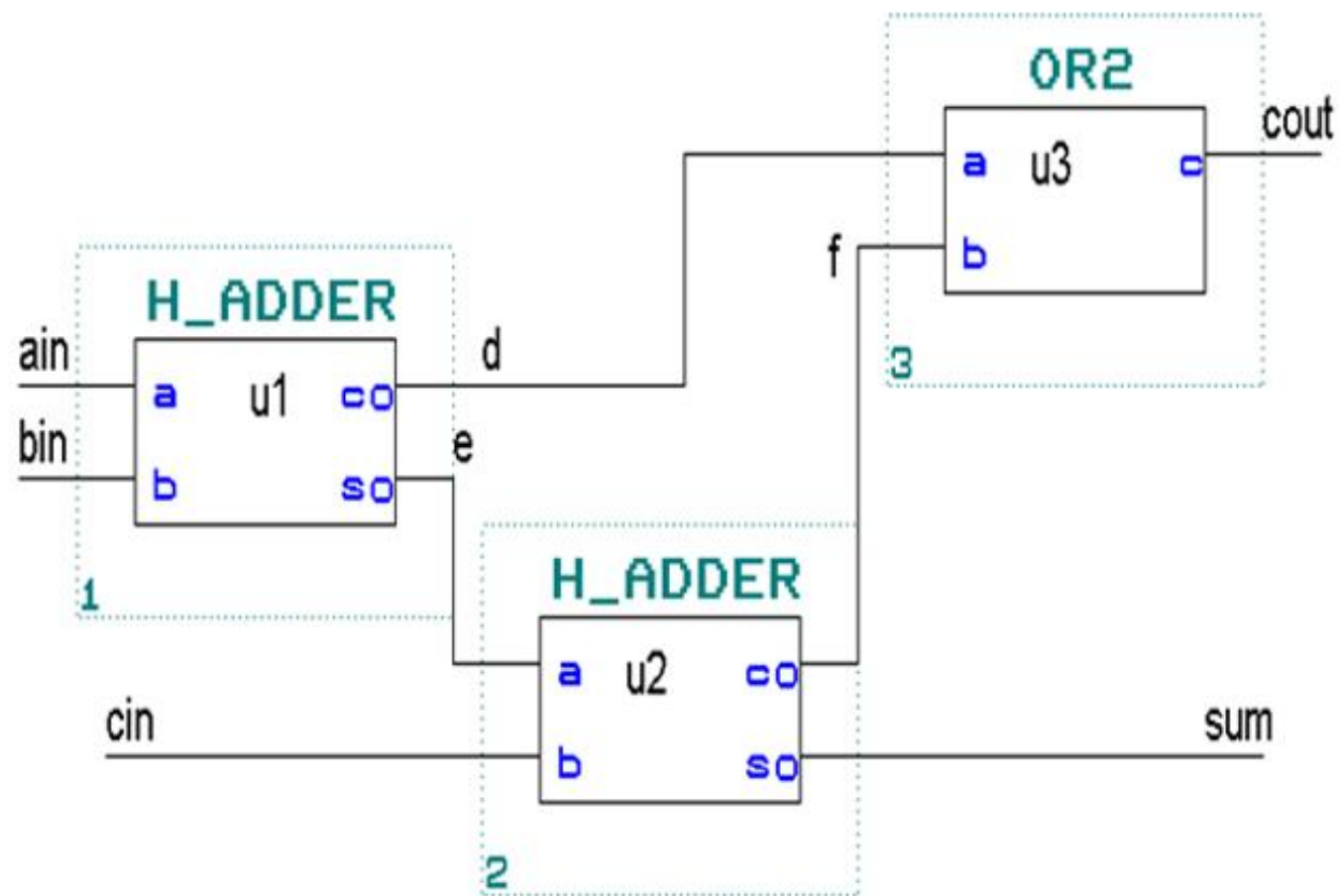

```
LIBRARY IEEE ;--或门逻辑描述
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY or2a IS
    PORT (a, b :IN STD_LOGIC;
          c : OUT STD_LOGIC );
END or2a ;
ARCHITECTURE art1 OF or2a IS
    BEGIN
        c <= a OR b ;
END art1;
```

```
LIBRARY IEEE; --半加器描述
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY h_adder IS
    PORT (a, b : IN STD_LOGIC;
          co, so : OUT STD_LOGIC);
END h_adder;
ARCHITECTURE art2 OF h_adder is
    BEGIN
        so <= a XOR b ;
        co <= a AND b ;
END art2;
```

--1位二进制全加器顶层设计描述

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
ENTITY f_adder IS
    PORT (ain, bin, cin : IN STD_LOGIC;
          cout, sum    : OUT STD_LOGIC );
```

```
END f_adder;
```

```
ARCHITECTURE art3 OF f_adder IS
```

```
    COMPONENT h_adder
        PORT ( a, b : IN STD_LOGIC;
              co, so : OUT STD_LOGIC);
    END COMPONENT ;
```

```
    COMPONENT or2a
        PORT (a, b : IN STD_LOGIC;
              c : OUT STD_LOGIC);
    END COMPONENT;
```

```
SIGNAL d, e, f : STD_LOGIC;
```


```
BEGIN
```

```
    u1 : h_adder PORT MAP (ain, bin, d, e);
```


```
    u2 : h_adder PORT MAP (a=>e, b=>cin, co=>f, so=>sum);
```

```
    u3 : or2a PORT MAP (d, f, cout);
```

```
END art3;
```

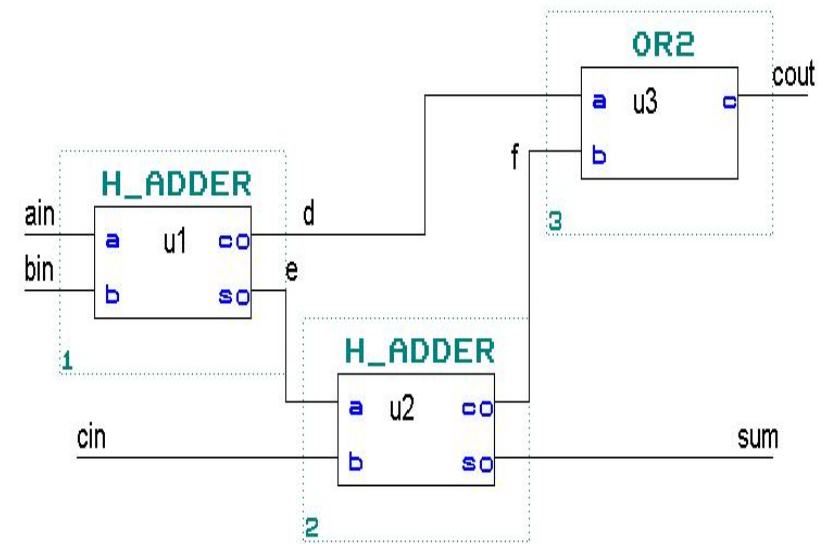

必须与元件例化中的端口顺序一致

 

VHDL 举例

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

```

4进制格雷码可逆计数器 X=0时顺时针

```


ENTITY count4 IS
    PORT ( clk , x : IN STD_LOGIC;
          qout : OUT STD_LOGIC_VECTOR (1 DOWNT0 0);
          y: OUT STD_LOGIC );
END count4;

```


```

ARCHITECTURE behv OF count4 IS
    TYPE state IS (s0, s1, s2, s3);
    SIGNAL c_state, n_state : state;
BEGIN
    REG: PROCESS (clk)
    BEGIN
        IF (clk' EVENT and clk='1' ) THEN
            c_state <= n_state;
        END IF ;
    END PROCESS;



```

 

```
COM:PROCESS (c_state, x)
  BEGIN
    CASE c_state IS
      WHEN s0 => qout <= "00" ;
        IF x = '0' THEN
          n_state <= s1;
          y <= '0';
        ELSE
          n_state <= s3;
          y <= '1';
        END IF;
      WHEN s1 => qout <= "01" ;
        IF x = '0' THEN
          n_state <= s2;
          y <= '0';
        ELSE
          n_state <= s0;
          y <= '0';
        END IF;
```

 

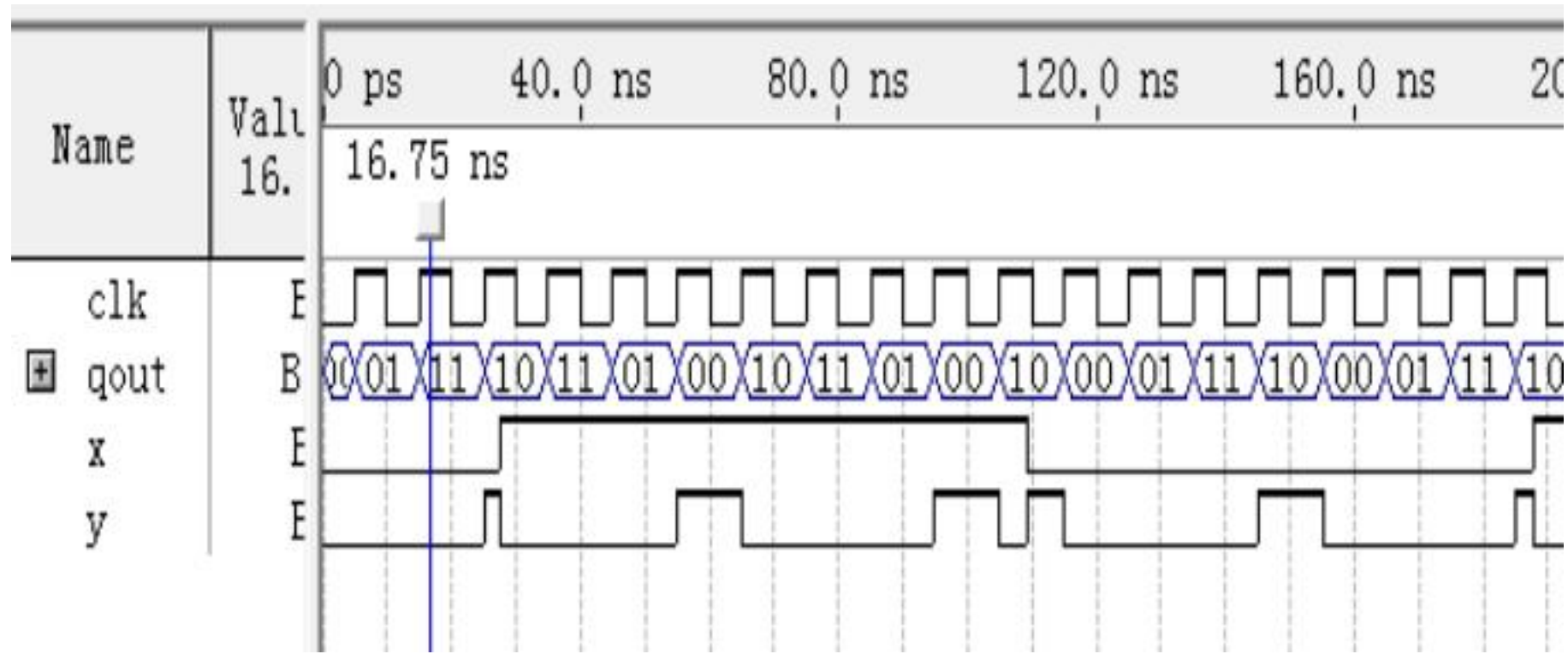 
```
    WHEN s2 => qout <= "11" ;
      IF x = '0' THEN
        n_state <= s3;
        y <= '0';
      ELSE
        n_state <= s1;
        y <= '0';
      END IF;
    WHEN s3 => qout <= "10" ;
      IF x = '0' THEN
        n_state <= s0;
        y <= '1';
      ELSE
        n_state <= s2;
        y <= '0';
      END IF;
    END case;
  END PROCESS;
END behv;
```




可编程逻辑器件器件的开发流程


开发工具

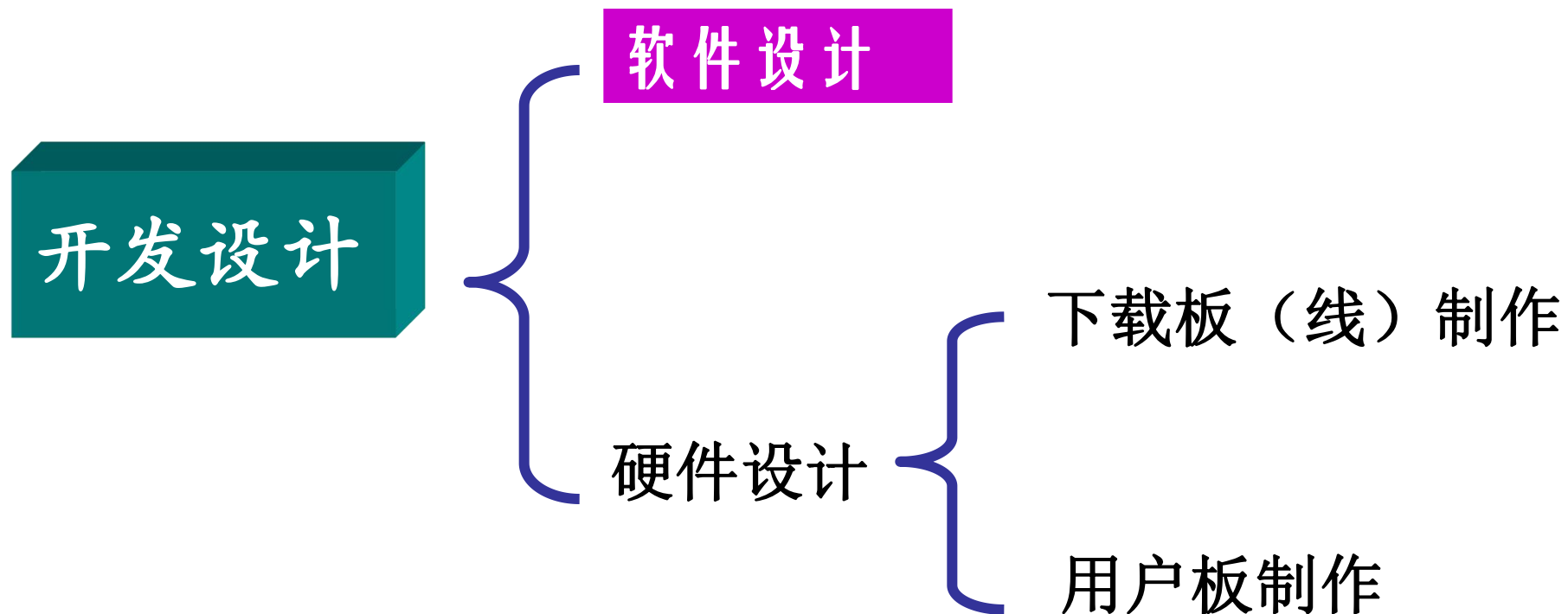

三、软件设计流程

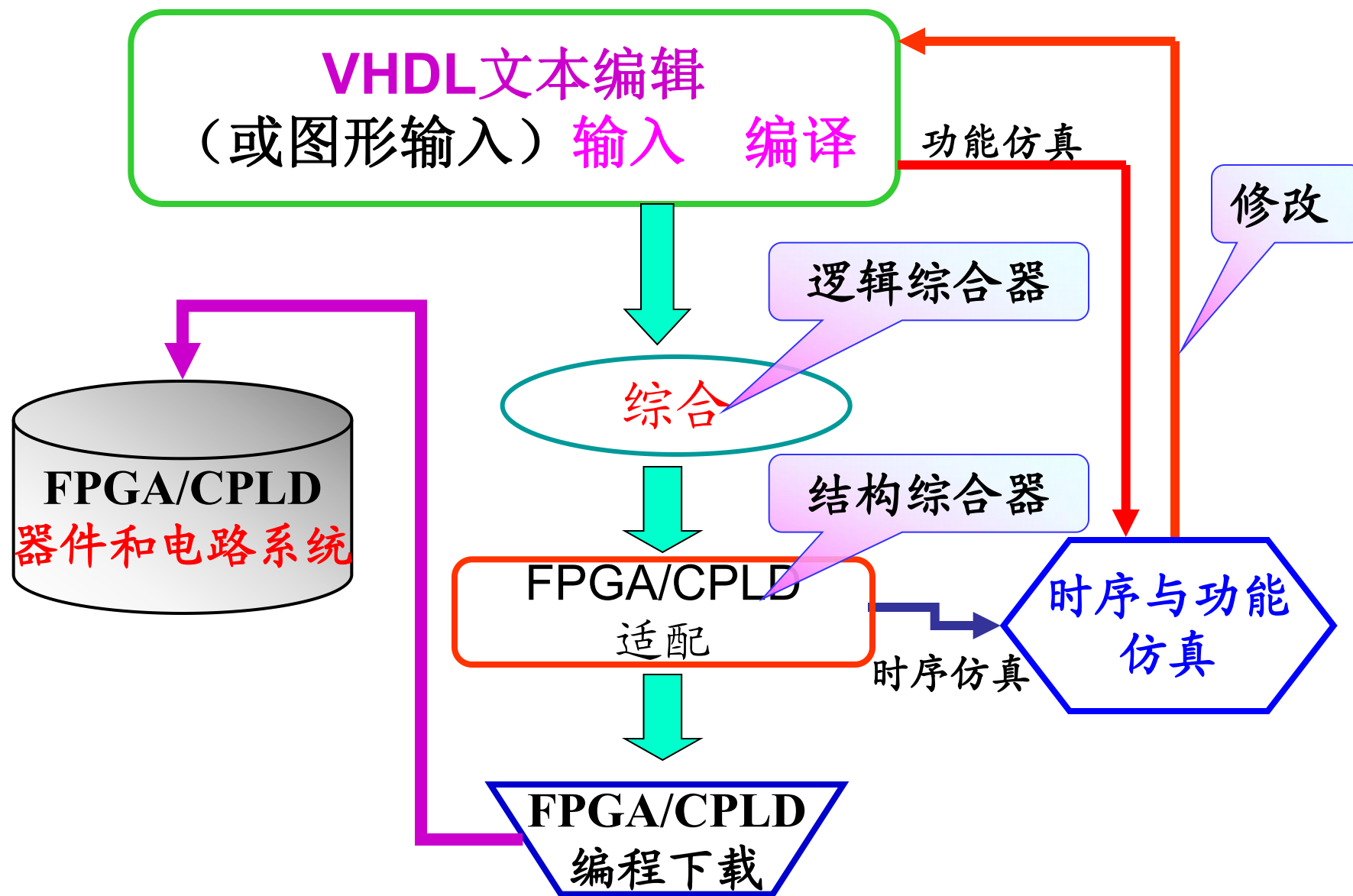

四.下载芯片（编程）

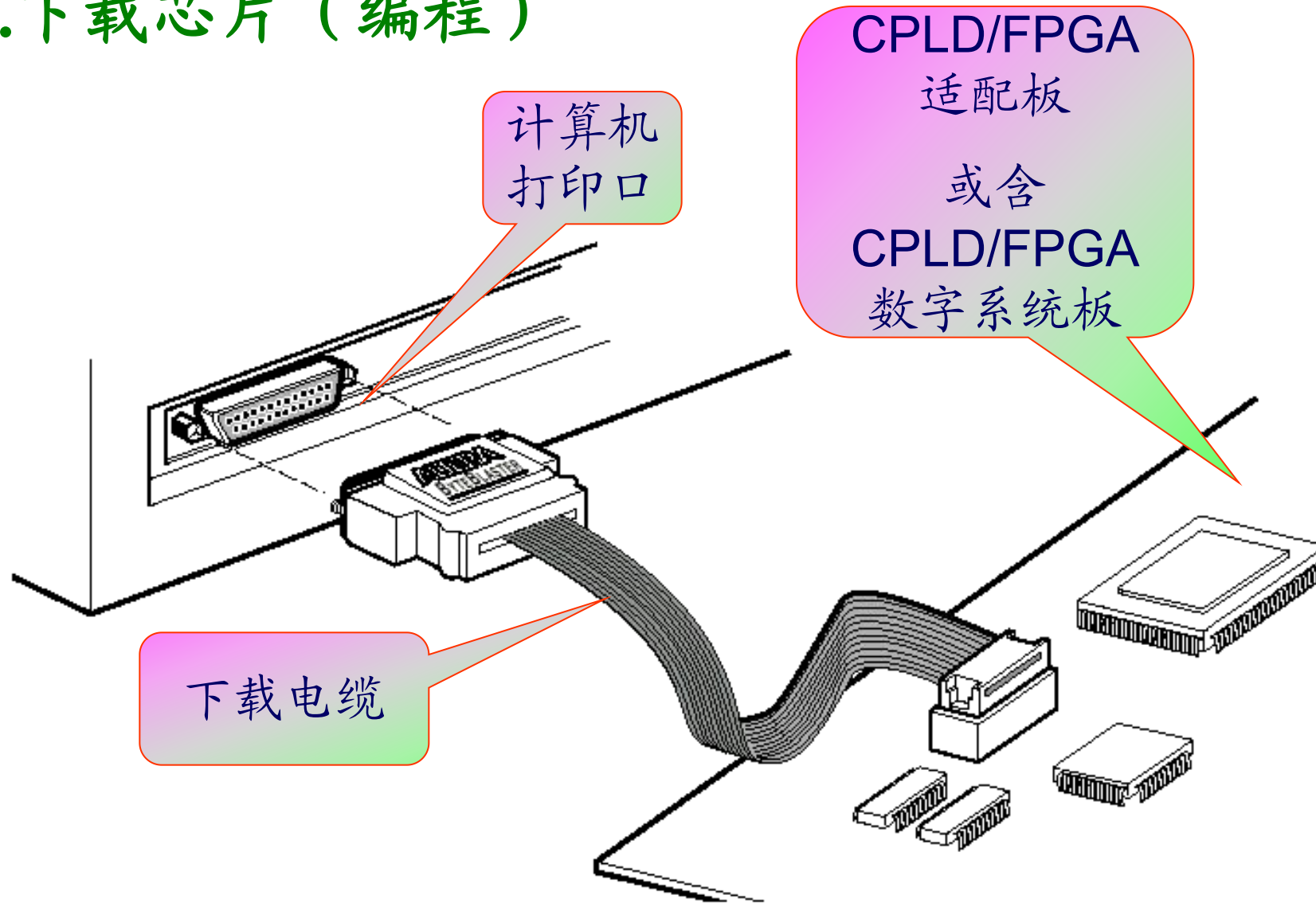

8个彩灯，4花样自动切换的彩灯控制器：

第1：从右到左，然后从左到右逐次点亮，再全黑，再全亮；

第2：两边同时亮1个逐次向中间移动再散开；

第3：两边同时亮2个逐次向中间移动再散开；

第4：每三个亮、每四个亮、间隔亮。

共32个种变换，循环往复。

Library ieee;

USE IEEE.STD_LOGIC_1164.ALL;

USE IEEE.STD_LOGIC_unsigned.ALL;

entity caideng is

Port (clk:in std_logic;

q:out std_logic_vector(7 downto 0));

end;

architecture art of caideng is

signal s:std_logic_vector(4 downto 0);

Begin

process (clk)

```
begin
  if clk'event and clk='1' then
    if s = 31 then
      s<="00000";
    else
      s<=s+1; --不用判断
    end if;
  end if;
end process;
```

process (s)

```
begin
case s is
  when "00000"=>q<="000000001";
  when "00001"=>q<="000000010";
  when "00010"=>q<="00000100";
  when "00011"=>q<="00001000";
  when "00100"=>q<="00010000";
  when "00101"=>q<="00100000";
  when "00110"=>q<="01000000";
  when "00111"=>q<="10000000";
```

```
  when "01000"=>q<="10000000";
  when "01001"=>q<="01000000";
  when "01010"=>q<="00100000";
  when "01011"=>q<="00010000";
  when "01100"=>q<="00001000";
  when "01101"=>q<="00000100";
  when "01110"=>q<="00000010";
  when "01111"=>q<="00000001";
  when "10000"=>q<="00000000";
  when "10001"=>q<="11111111";
  when "10010"=>q<="10000001";
  when "10011"=>q<="01000010";
  when "10100"=>q<="00100100";
  when "10101"=>q<="00011000";
  when "10110"=>q<="00100100";
  when "10111"=>q<="01000010";
  when "11000"=>q<="10000001";
  when "11001"=>q<="11000011";
  when "11010"=>q<="00111100";
```

```
when "11011"=>q<="11000011";  
when "11100"=>q<="11100111";  
  when "11101"=>q<="11110000";  
when "11110"=>q<="00001111";  
when "11111"=>q<="01010101";  
when others=>null;  
end case;  
end process;  
End art;
```

序列信号发生器如何实现?
顺序脉冲发生器如何实现?